

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018**

**Course Code: EC201**

**Course Name: NETWORK THEORY**

Max. Marks: 100


Duration: 3 Hours

**PART A**


*Answer any two full questions, each carries 15 marks.*

Marks

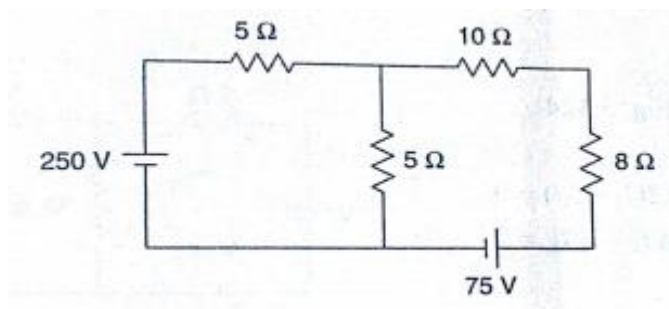
- 1 a) State and prove initial value theorem and final value theorem (8)
- b) Find the current through  $8\ \Omega$  resistor in the network using Thevenin's theorem (7)



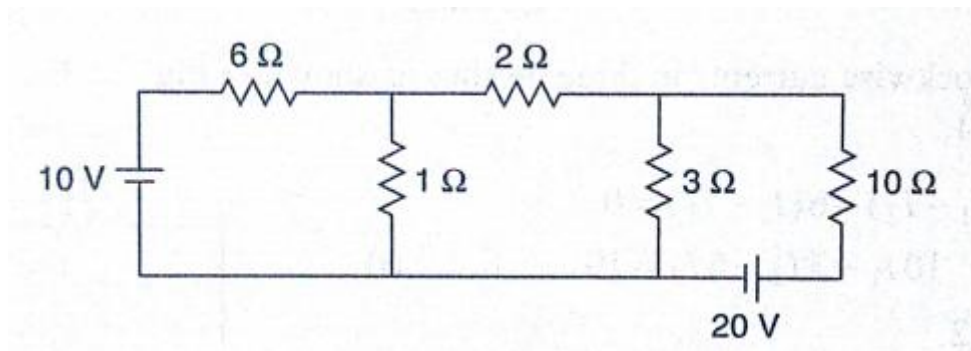- 2 a) Find the current through  $2\ \Omega$  resistor using Mesh analysis (8)



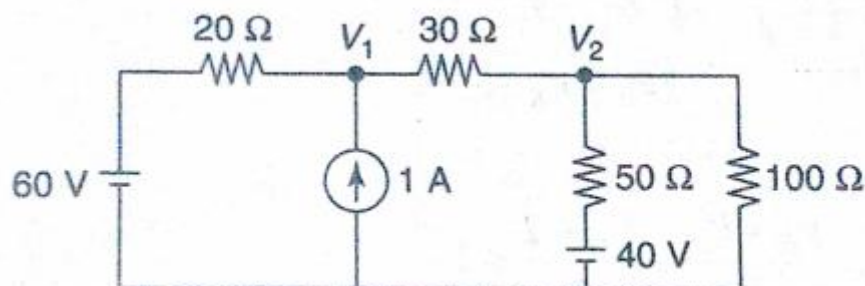
- b) Find the current in the  $100\ \Omega$  resistor using Nodal analysis (7)



- 3 a) State and prove maximum power transfer theorem when the load impedance is a (8)

complex impedance with variable resistance and variable reactance

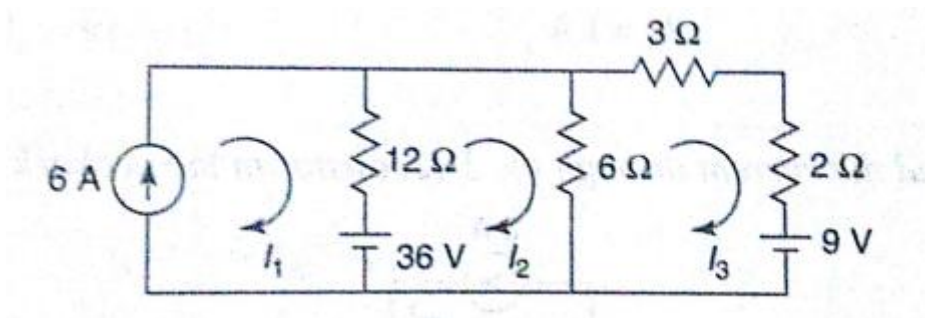- b) Find the current through the  $2\ \Omega$  resistor (7)




### PART B


*Answer any two full questions, each carries 15 marks.*

- 4 a) Solve  $\frac{dy}{dt} + 2y = e^{-3t}$ ,  $y(0) = 1$  (8)

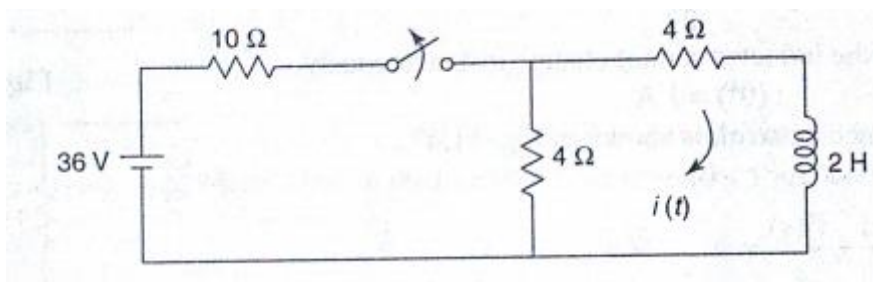
- b) The network shown has acquired steady state with the switch closed for  $t < 0$ . At  $t = 0$ , the switch is opened. Obtain  $i(t)$  for  $t > 0$ . (7)



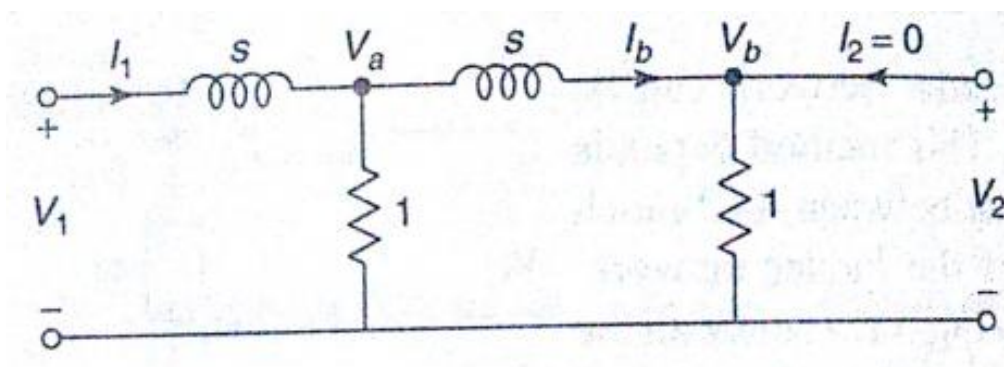
- 5 a) For the network determine the voltage transfer function  $V_2/V_1$  (7)



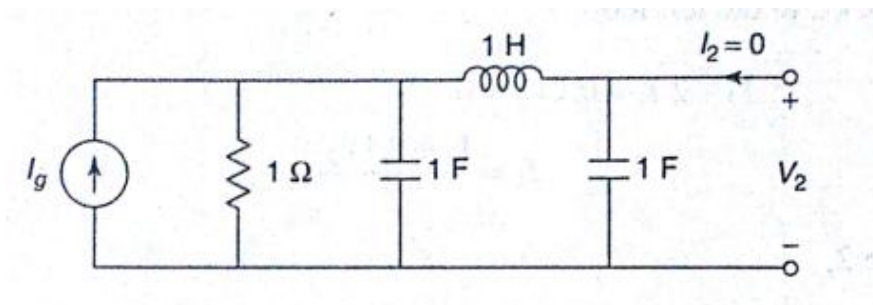
- b) For the network shown determine  $V_2/I_g$ . Plot the pole zero diagram of  $V_2/I_g$ . (8)



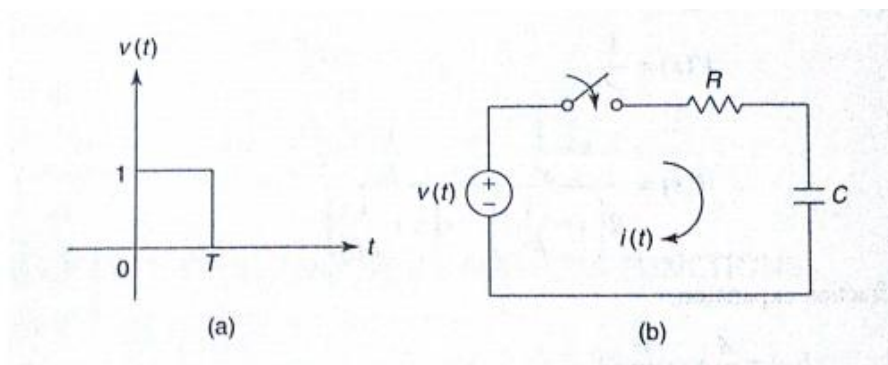- 6 a) A rectangular voltage pulse of unit height and  $T$  second duration is applied to a series RC network at  $t=0$ . Obtain the expression for current  $i(t)$ . Assume the capacitor to be initially uncharged. (7)



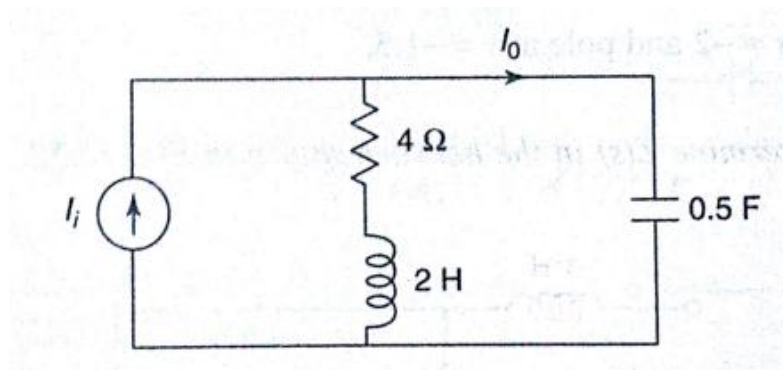
- b) For the network shown plot poles and zeros of function  $I_0/I_i$  (8)



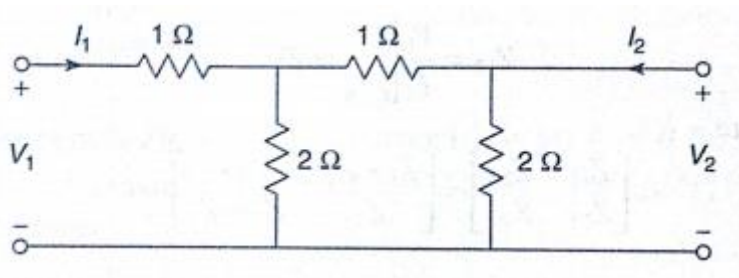
## PART C

*Answer any two full questions, each carries 20 marks.*

- 7 a) Find Z parameters for the network shown (10)



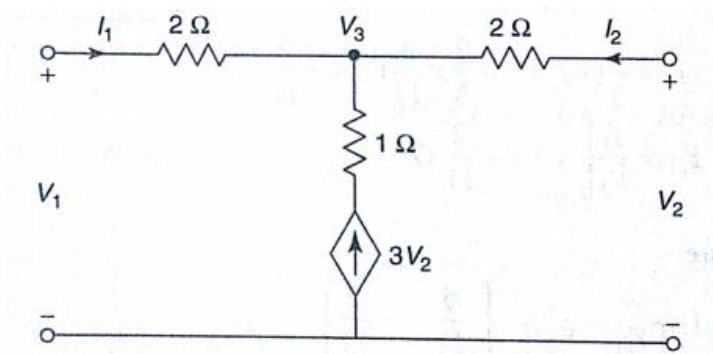- b) Find the Y parameters of the network shown (10)



- 8 a) Derive the resonance frequency for a series RLC circuit and give its power factor, current and voltage at resonance (10)
- b) A series RLC circuit has a quality factor of 5 at 50 rad/s. The current flowing through the circuit at resonance is 10 A and the supply voltage is 100 V. Find the circuit constants R, L and C (10)
- 9 a) Compare series and parallel resonant circuits (current, impedance, power factor, resonant frequency and Q factor) (10)
- b) A coil of 10  $\Omega$  resistance and 2 H inductance is connected in parallel with a variable capacitor across a 220 V, 50 Hz supply. Calculate (a) the capacitance of the capacitor for the resonance, (b) the dynamic impedance of the circuit and (c) supply current (10)

\*\*\*\*\*

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

THIRD SEMESTER B.TECH DEGREE EXAMINATION(S), MAY 2019

**Course Code: EC201****Course Name: NETWORK THEORY**


Max. Marks: 100

Duration: 3 Hours

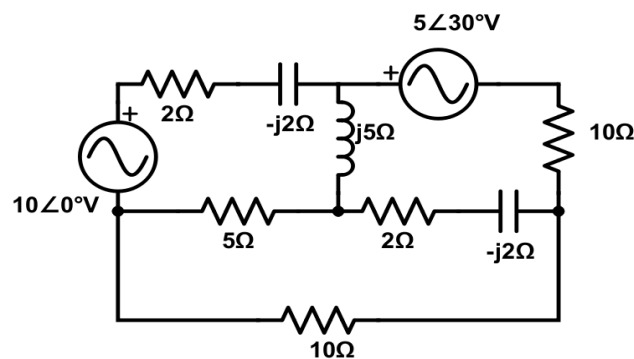
**PART A***Answer any two full questions, each carries 15 marks.*

Marks


- 1 a) Find the voltage across  $10\Omega$  resistor using mesh analysis. (8)



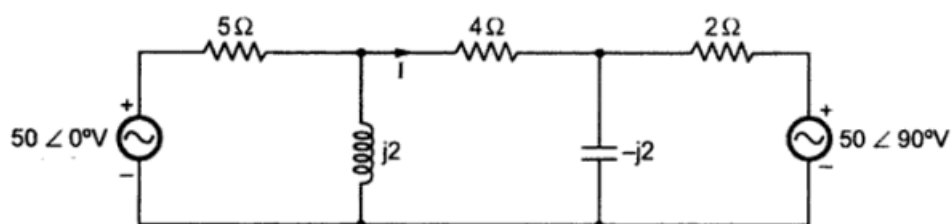
- b) State and prove the following properties of Laplace transform i) Time Shifting ii) Frequency Shifting (7)
- 2 a) Find current  $I$  using node analysis. (8)



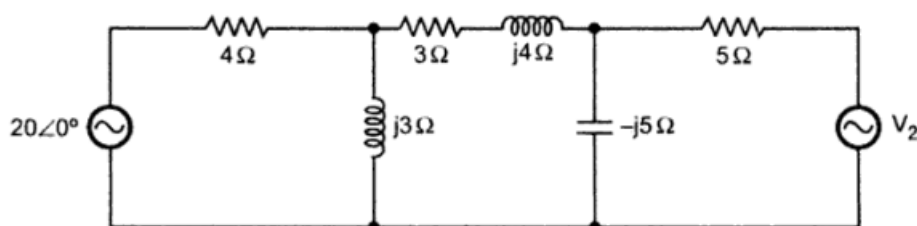
- b) Determine the value of  $V_2$  such that the current through the impedance  $(3+j4)\Omega$  is zero. (7)



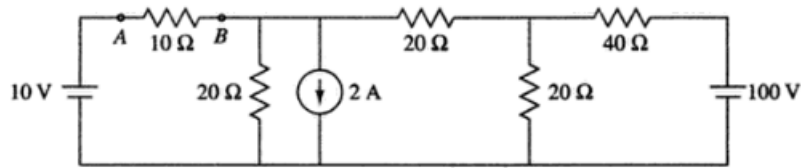- 3 a) Determine the voltage across  $10\Omega$ , connected between the terminals A and B, using superposition theorem. (9)



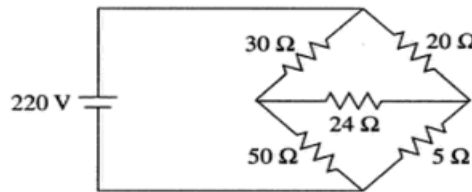
- b) Using Thevenin's theorem, find the power dissipated across  $24\Omega$  resistor. (6)



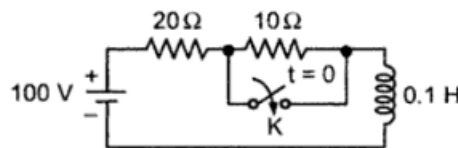
### PART B

*Answer any two full questions, each carries 15 marks.*

- 4 a) Obtain the transient current and voltage responses of a RL circuit when subjected to a unit step input. (6)
- b) Solve the differential equation  $\frac{d^2v(t)}{dt^2} + 6\frac{dv(t)}{dt} + 8v(t) = 2u(t)$  subject to the initial conditions  $v(0) = 1, v'(0) = -2$ . (9)
- 5 a) For the given network function, draw the pole-zero plot and hence, obtain its time domain response from the plot.  $V(s) = \frac{5(s+5)}{(s+2)(s+7)}$  (8)
- b) A dc voltage of 100V is applied in the circuit shown in the figure and the switch, K is kept open. The switch is closed at  $t=0$ . Find the resulting current. (7)



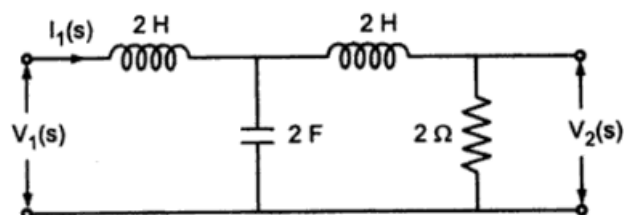
- 6 a) Write down the necessary conditions for driving point functions. (6)
- b) For the network shown, find the following  $\frac{I_2(s)}{I_1(s)}, \frac{V_2(s)}{V_1(s)}$  and  $\frac{V_1(s)}{I_1(s)}$ . (9)



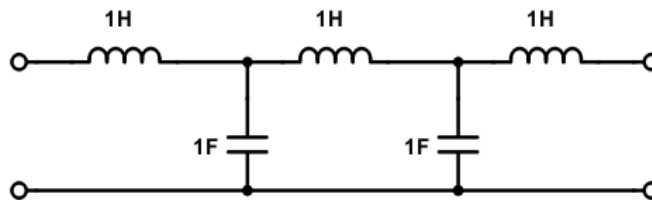
## PART C

Answer any two full questions, each carries 20 marks.


- 7 a) Show that the overall Y parameter, of two 2-port networks when connected in parallel, is the sum of individual Y parameters of the two networks. (6)
- b) Determine the transmission parameters of the two port network given below. (9)



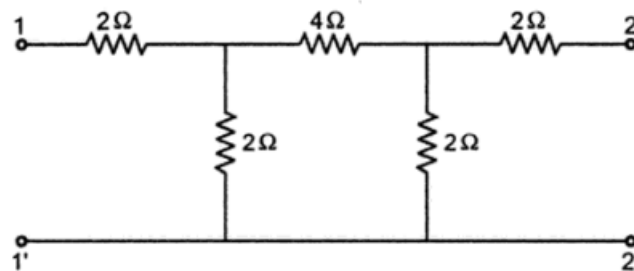- c) Define the terms (i) Characteristic impedance (ii) Propagation Constant (5)
- 8 a) A series RLC circuit resonates at a frequency of 1500Hz and consumes 75W power for 50V ac source at resonant frequency. The bandwidth is 0.75kHz. Calculate R, L and C. Also calculate the maximum current and half power frequencies. (10)
- b) Obtain the open circuit Z parameters of the network shown in figure. (10)



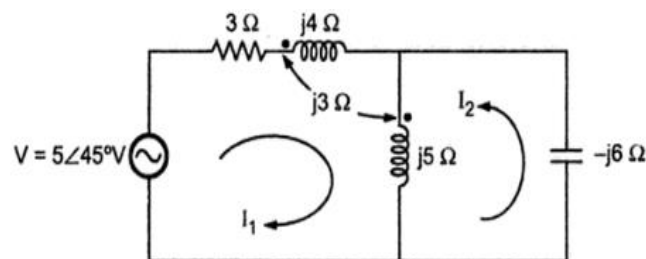- 9 a) Derive the expressions for (i) maximum output voltage and (ii) maximum amplification factor for a single tuned circuit. (12)
- b) Find the drop across the capacitor. (8)



\*\*\*\*

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**THIRD SEMESTER B.TECH DEGREE EXAMINATION(R&S), DEC 2019**

**Course Code: EC201**

**Course Name: NETWORK THEORY**

Max. Marks: 100


Duration: 3 Hours

**PART A**

*Answer any two full questions, each carries 15 marks.*


Marks

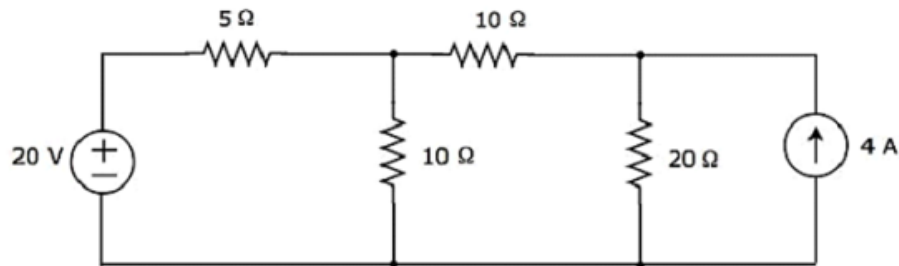- 1 a) Classify independent and dependent sources. Also mention the types of dependent sources. (4)
- b) Calculate the current through  $20\Omega$  using node analysis (4)




fig(1)

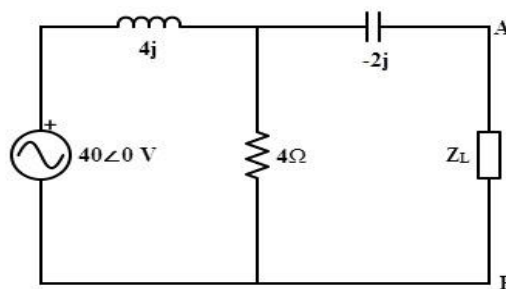- c) Find the value of load and maximum power delivered to load in fig(2) (7)



fig(2)

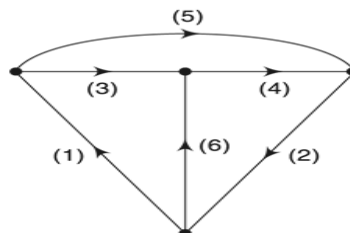
- 2 a) Find the tie set matrix for the graph shown in fig(3) (4)



fig(3)




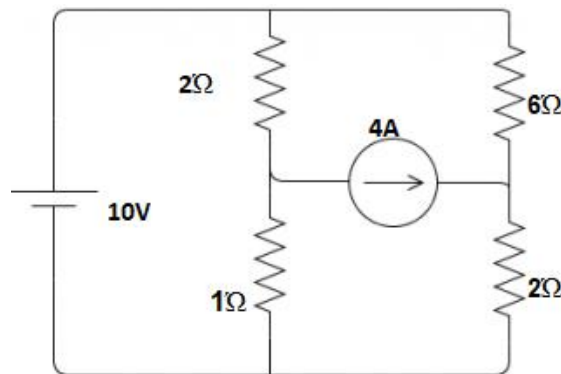- b) Define Node, Tree and Link (3)
- c) State and prove initial value and final value theorem (8)
- 3 a) Solve the circuit and find the loop currents in fig(4) (6)



fig(4)

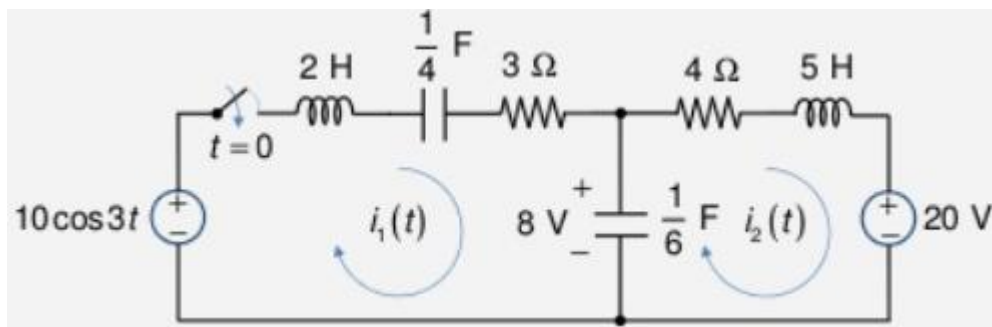- b) State reciprocity theorem (3)
- c) Draw the laplace transformed circuit and write the mesh equations for the circuit shown in fig(5) (6)




fig(5)
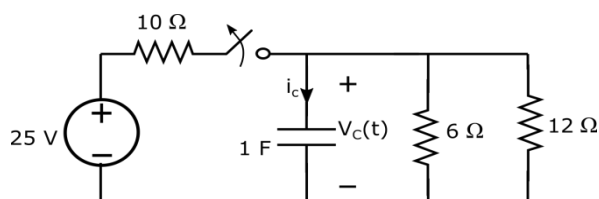
### PART B

*Answer any two full questions, each carries 15 marks.*

- 4 a) Find the inverse laplace transform of (8)
- $$F(s) = \frac{21s - 33}{(s + 1)(s - 2)^3}$$
- b) Write any six properties of driving point and transfer functions. (7)
- 5 a) The switch is opened at  $t = 0$ . Find the capacitor voltage for  $t > 0$  (8)




fig(6)

- b) Draw the pole zero diagram of system function  $\frac{S^3 - 7S^2 + 10S}{S^2 + S - 6}$ . Also mention the nature of the system. (7)
- 6 a) Solve the differential equation using laplace transform (7)
- $$2y'' + 3y' - 2y = te^{-2t}, \quad y(0) = 0 \quad y'(0) = -2$$
- b) Draw Pole Zero Plot & using pole zero plot, Find the time domain response i(t). (8)
- $$I(S) = \frac{2S}{(S+2)(S^2 + 2S + 2)}$$
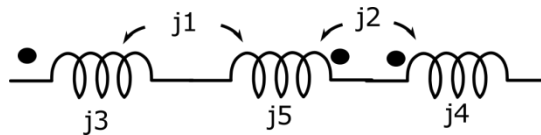
### PART C


*Answer any two full questions, each carries 20 marks.*

- 7 a) The Z parameters of a two port network are  $Z_{11}=20\Omega$ ,  $Z_{12}=Z_{21}=10\Omega$ ,  $Z_{22}=30\Omega$ . Find Y and ABCD parameters. (9)
- b) Derive the expression for voltage amplification of single tuned circuits. (7)
- c) Find the equivalent inductance (4)




fig(7)

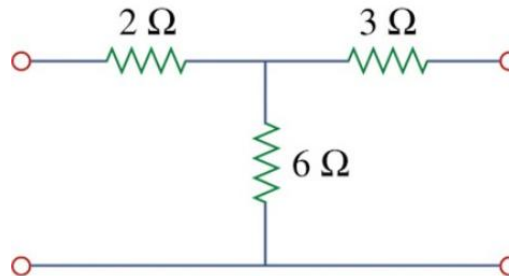- 8 a) Find the hybrid parameters for the network in fig(8). Also represent its hybrid model. (6)




fig(8)

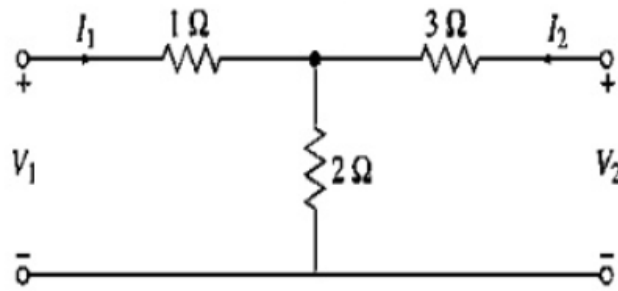- b) Explain characteristics impedance and image impedances (6)
- c) Find the expressions for resonant frequency, Q factor and bandwidth of parallel RLC network (8)
- 9 a) Find the Y parameters of the circuit shown and comment on the symmetry and reciprocity of the circuit. (7)



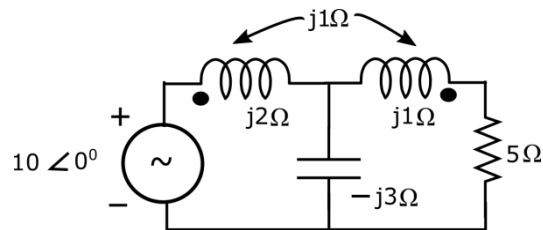- b) For the circuit shown, find the drop across  $5\ \Omega$  (7)



- c) Compare and classify parallel resonance network and series resonance network (6)

\*\*\*\*

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

Third semester B.Tech examinations (S) September 2020

**Course Code: EC201****Course Name: NETWORK THEORY**


Max. Marks: 100

Duration: 3 Hours

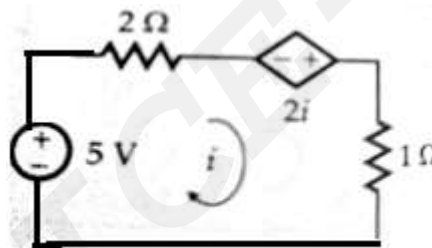
**PART A***Answer any two full questions, each carries 15 marks.*

Marks

- 1 a) Explain Kirchoff's law with example (2)
- b) Explain final value theorem. Find final value of  $F(s) = \frac{2}{s} - \frac{1}{s+3}$  (8)
- c) Find the value of dependent voltage source (5)



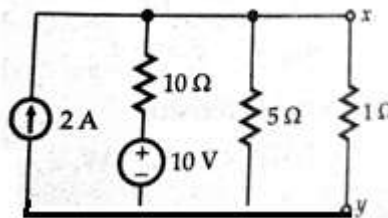- 2 a) Find the power loss in 1 Ω resistor by Thevenin's theorem (8)



- b) Explain maximum power transfer theorem applied to dc circuits (7)
- 3 a) Find the Laplace transform of (i)  $f(t) = \cos^3 3t$  and (ii)  $f(t) = \frac{(1-e^{-t})}{t}$  (8)
- b) Explain tie set matrix, cut set matrix and fundamental cut set matrix with an example (7)

**PART B***Answer any two full questions, each carries 15 marks.*

- 4 a) A continuous LTI system is initially relaxed and represented by the equation  $y''(t) + 3y'(t) + 2y(t) = 2x(t)$ . Using Laplace transform Find (a) transfer (8)

- function and (b) Find response of a system for input  $x(t) = 4 e^{-3t}$
- b) A series RLC circuit with  $R = 100\Omega$ ,  $L = 0.1 \text{ H}$  and  $C = 40 \mu\text{F}$  has a dc voltage of 200 V applied at  $t = 0$ . Find the transient current. (7)
- 5 a) Derive the response of a series RC circuit for a step input (5)
- b) What are the restrictions on poles and zeros for the transfer function and driving point functions (10)
- 6 a) A  $100\mu\text{F}$  capacitor has an initial charge  $Q_0 = 0.002 \text{ C}$  is connected in series with  $200\Omega$  across 50V supply at time  $t = 0$ . Find the transient current. (8)
- b) Define poles and zeros of a transfer function. For the given transfer function find the poles and zeros and also draw the pole zero plot (7)
- $I(s) = 20(s+5) / (s^2 + 5s + 6)$

### PART C

*Answer any two full questions, each carries 20 mark.*

- 7 a) Two inductively coupled coils have self-inductance  $L_1 = 50\text{mH}$ ,  $L_2 = 200\text{mH}$ . Given  $k = 0.5$ . Find the mutual inductance between the coil (3)
- b) Two coupled coils have a coefficient of coupling  $k = 0.83$ . With coil 1 open, a current of 5A flows in coil 2. Given flux in coil 2 is 0.35 milli weber. Find  $L_1$ ,  $L_2$  and  $M$ . (6)
- c) A coil having an inductance and resistance of 50 mH and  $100\Omega$  is connected in series with a capacitor and a 100V, 1 kHz source. Find the value of capacitance that will cause resonance in the circuit. Find the resulting current at resonance (6)
- d) Define characteristic impedance and image impedance (5)
- 8 a) Explain Y parameters. (6)
- b) Derive the inter relation between open circuit impedance parameters and transmission parameters (6)
- c) In a RLC series circuit, the resistance, inductance and capacitance are  $10\Omega$ , 100 mH and  $10 \mu\text{F}$ . Find  $\omega_0$ ,  $\omega_1$  and  $\omega_2$ . Also find band width and selectivity (8)
- 9 a) Explain parallel inter connection of two port networks (6)
- b) The h parameters of a two port network are  $h_{11} = 1.5 \text{ k}\Omega$ ,  $h_{12} = 2 \times 10^{-3}$ ,  $h_{21} = 250$  and  $h_{22} = 150 \times 10^{-6}$ . Find Z parameters and draw its equivalent (7)
- c) Explain Double tuned coupled coils (7)

\*\*\*\*